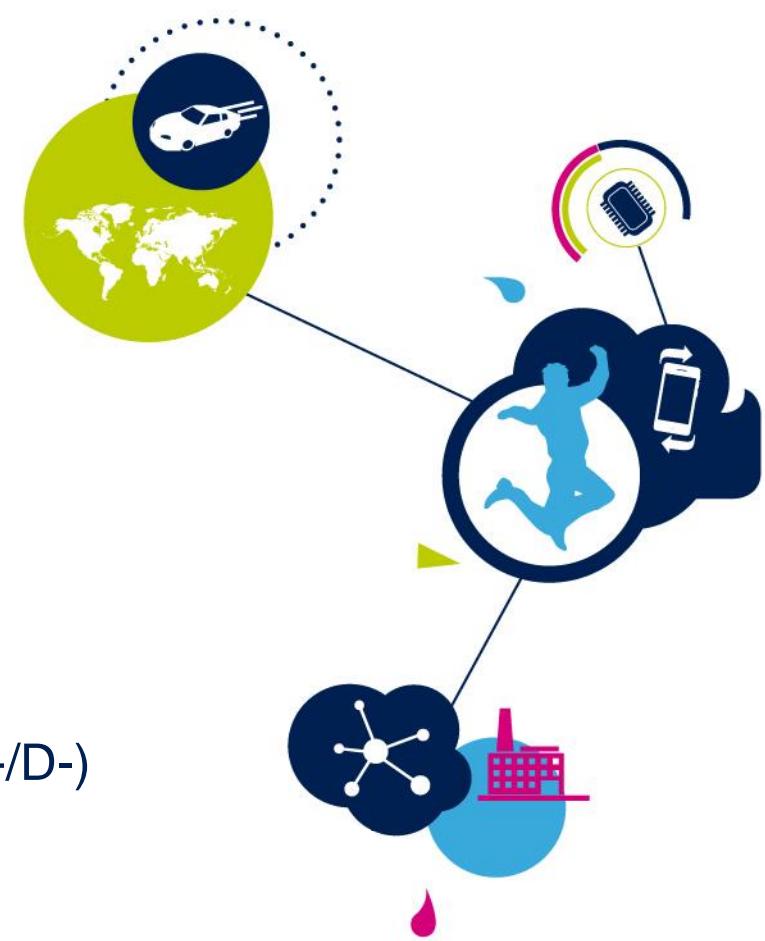


USB-C PD controllers Power + Data

Examples implementing USB-C Power (Vbus) with USB2.0 Data (D+/D-)







USB Type-C + USB 2.0

2

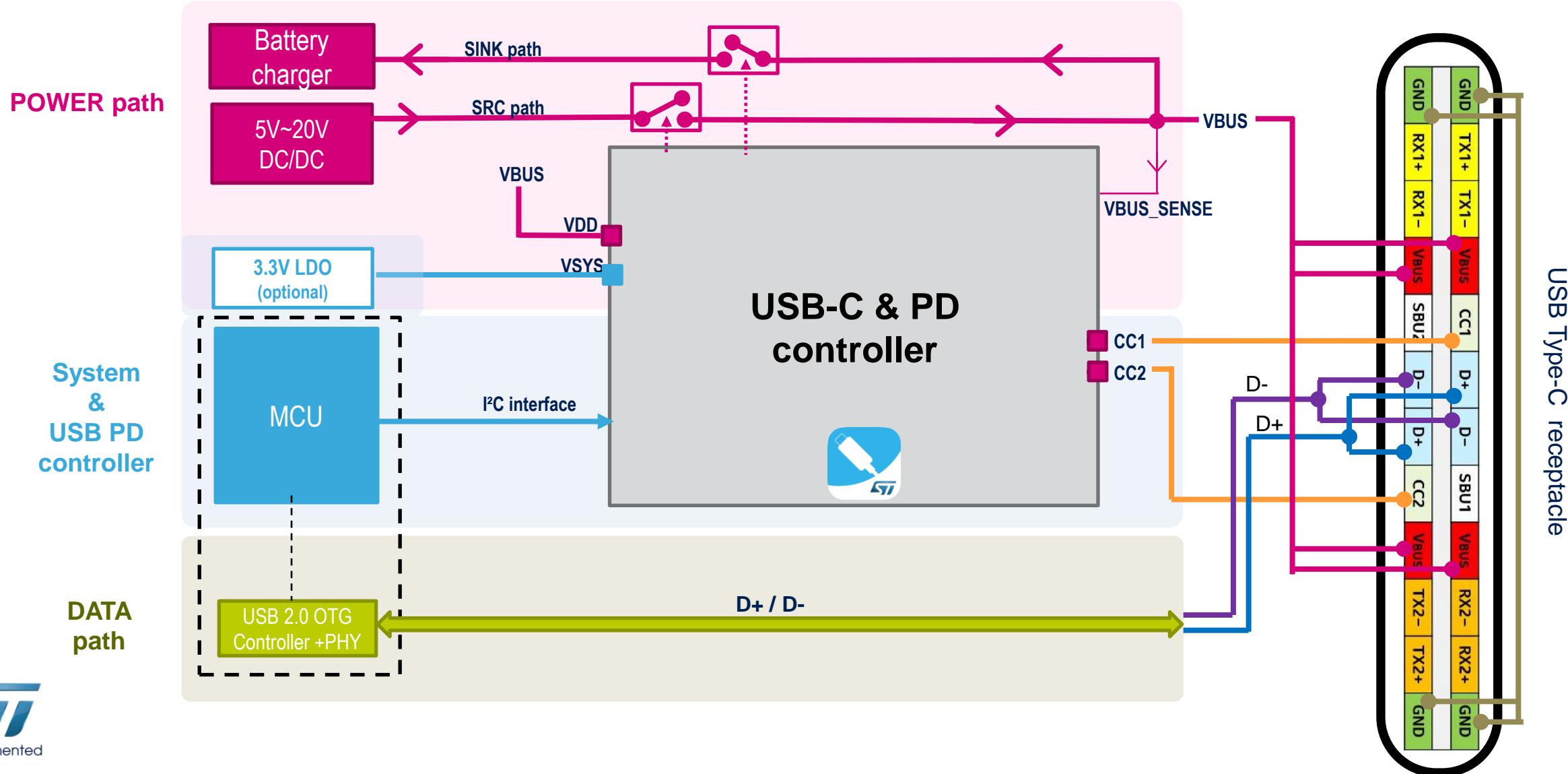HW implementation in Dual Role (DRP) mode




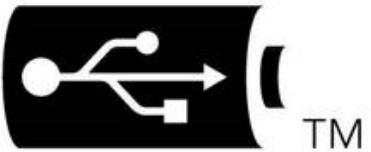

USB-C PD SINK + USB 2.0 Device

3

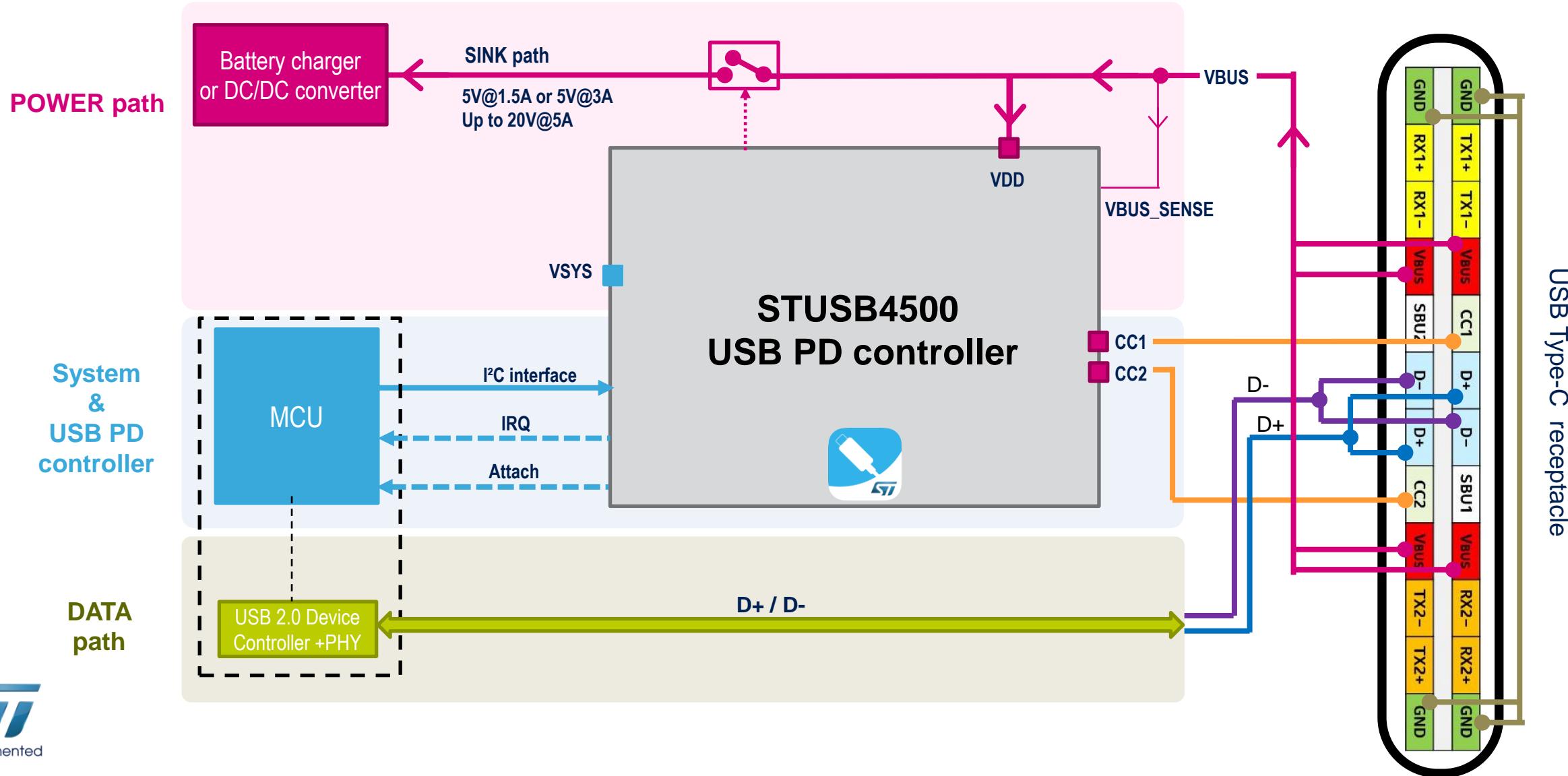HW implementation in Sink mode with STUSB4500






USB-C PD Source + USB 2.0 Host

HW implementation in SRC mode with STUSB4710

4

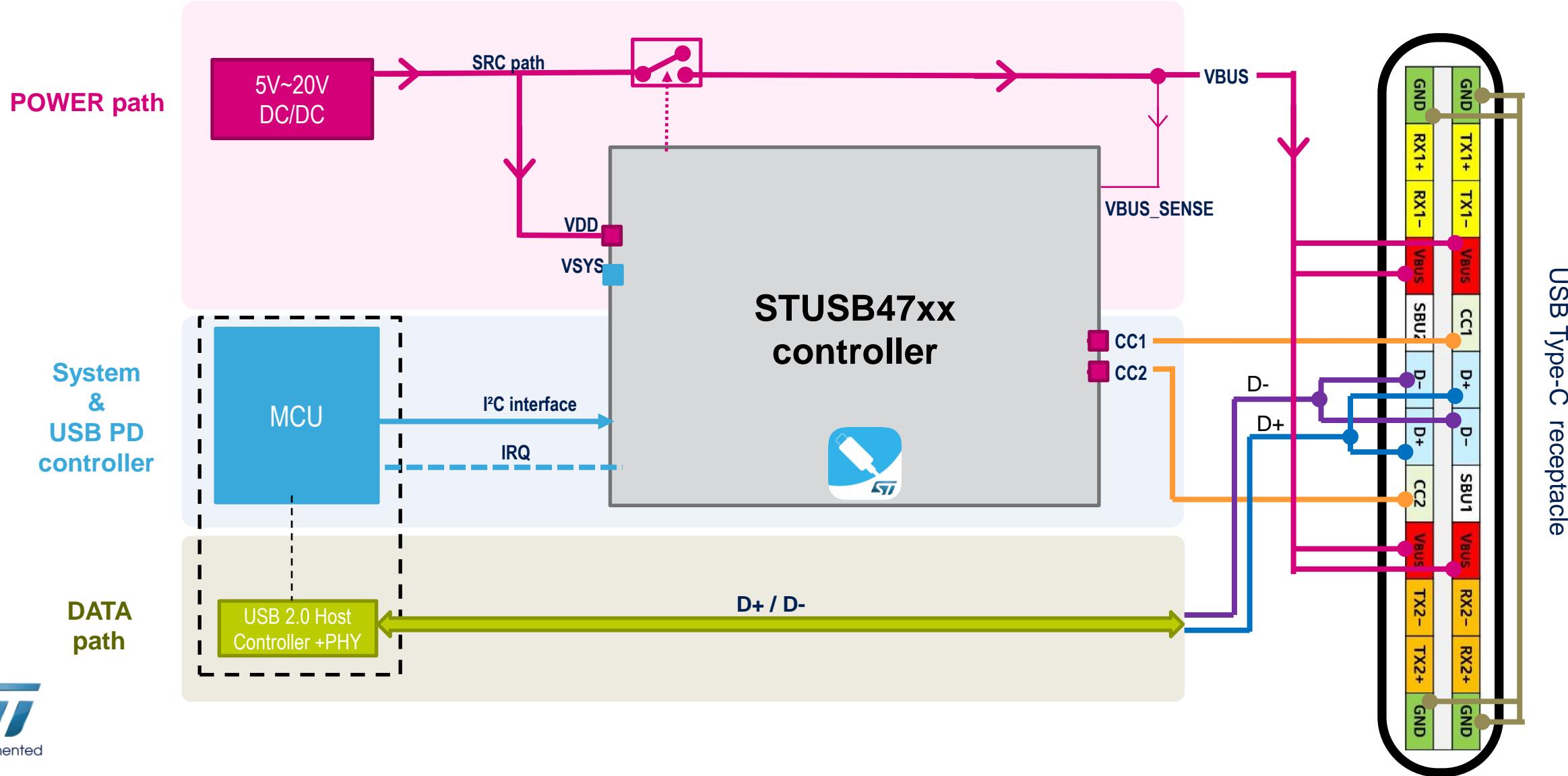

STUSB1602 Dual-Role Power (DRP)

5

Implementation example for Source and Sink

