



## Introduction

The M24LRxx ICs are a family of Dual Interface EEPROMs from STMicroelectronics. Each EEPROM IC can be accessed as a single memory bank via a wired or RF interface.

The RF interface:

- Is based on a passive RFID technology supporting the ISO15693 standard.
- Communicates with ISO15693 RF systems (called RFID readers),
- Does not require any on-board power to operate. Both energy and data are received from the RFID reader.

In order for the RF interface of the IC to operate, an inductive antenna is required. This antenna must be connected to the IC RF port.

There are three different methods for implementing an inductive antenna.

1. **On-board etched antenna:** this method consists of designing an on-board inductive antenna etched on the PCB itself. It allows for a wide range of antenna sizes but has a cost in terms of PCB real estate. Refer to the application note AN2972 *Designing an antenna for the M24LR64 dual interface I<sup>2</sup>C/RFID device* for guidance. ST also provides antenna templates in Gerber format.
2. **Off-board antenna module:** this method consists of using an external antenna, connected to the M24LR64, and to the main PCB through an I<sup>2</sup>C connector. This allows for a larger antenna, resulting in a greater read range. The off-board antenna can be made of:
  - a) A daughter board using simple PCB technology
  - b) A flexible antenna, equipped with an M24LRxx device and a wired I<sup>2</sup>C connection.
3. **External surface-mount inductor:** this consists of connecting an external inductor to the M24LRxx. This can have a small footprint and requires no design effort, but it has a reduced read range.

This application note provides guidelines for the third option: using an external surface-mount inductor as an RF antenna for M24LRxx ICs.

Contents

1      **Basic principle - inductance value** ..... 3

2      **Choosing the right type of surface-mount inductor** ..... 4

3      **Implementation** ..... 5

4      **ANT3-M24LR-A reference design** ..... 6


5      **Read range considerations** ..... 9

6      **Revision history** ..... 10



# 1 Basic principle - inductance value

Figure 1. M24LR64 dual interface EEPROM

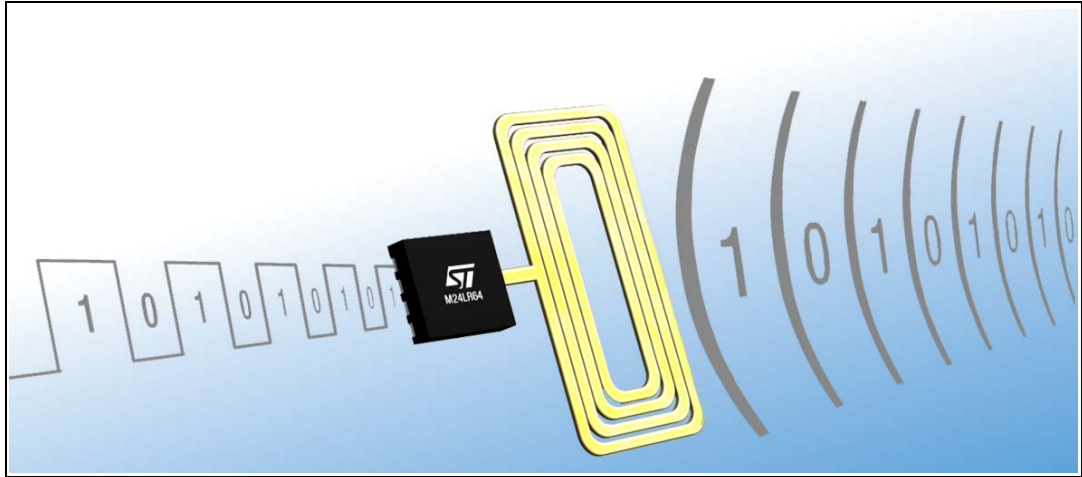

The basic principle of the M24LRxx's antenna is very simple: the external antenna inductance ( $L_{\text{INDUCTOR}}$ ) that needs to be integrated on the PCB should match the M24LRxx's internal tuning capacitor ( $C_{\text{TUNING\_IC}}$ ) in order to create a circuit resonating at 13.56 MHz. This is because ISO15693 RFID readers operate in the 13.56 MHz High Frequency band.

The equation is:

$$f_{\text{TUNING}} = \frac{1}{2\pi \times \sqrt{L_{\text{INDUCTOR}} \times C_{\text{TUNING\_IC}}}}$$

Which implies:

$$L_{\text{INDUCTOR}} = \frac{1}{(4 \times \pi^2 \times f_{\text{RESONANCE}}^2 \times C_{\text{TUNING\_IC}})}$$



This is how the inductance value is calculated:  $f_{\text{RESONANCE}} = 13.56$  MHz and in the case of an M24LRxx IC with an embedded 28 pF internal tuning capacitor, the theoretical value of the inductance is 4.92  $\mu\text{H}$ .

Refer to application note AN2972 *Designing an antenna for the M24LR64-R dual interface I<sup>2</sup>C/RFID device* for further information on the basics of the RFID technology, and for guidelines on antenna design, optimization and test.

## 2 Choosing the right type of surface-mount inductor

Because the inductor connected to the M24LRxx ICs is intended to capture the RF field from an external RFID reader, the coil of the selected inductor must not be shielded in order to be able to capture the emitted electromagnetic field. In other words, it must not be embedded inside any type of Faraday cage.


Table 1. Comparison of surface mount inductor types

Example of the right type of surface-mount inductor coil	Example of incorrect type of surface-mount inductor
	
<p>– No metal shield prevents it from capturing the electromagnetic field emitted by the RFID reader</p>	<p>– Coil is protected by a metal shield acting as a Faraday cage, disabling its capability to capture the electromagnetic field emitted by the RFID reader</p>

### 3 Implementation

To use an off-the-shelf inductor in your design, one option is to design the footprint of an optional external capacitor, in order to be able to fine-tune the antenna tuning frequency if needed.

**Figure 2. Possible implementation using an external inductor and an external tuning capacitor**

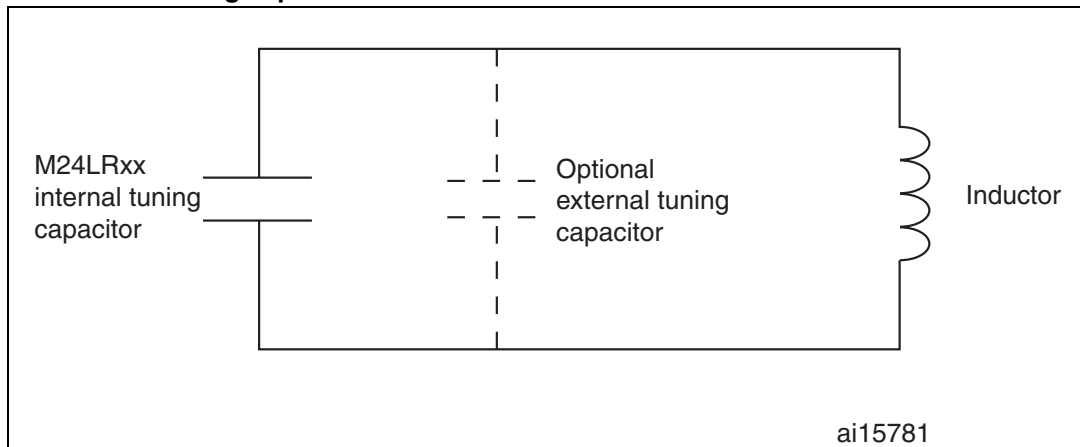

Refer to The application note AN2972 *Designing an antenna for the M24LR64-R dual interface I<sup>2</sup>C/RFID device* for further details on antenna design and optimization.

## 4 ANT3-M24LR-A reference design

ANT3-M24LR-A is a reference design proposed by ST as an example of using an external inductor.

The M24LR64-RMN6T/2 IC is installed on the ANT3-M24LR-A board. The external inductor's inductance value is 4.7  $\mu\text{H}$ , and no external tuning capacitor is installed.

Please contact your local sales and marketing office for further information about this reference design.

**Figure 3.**  $L_{\text{INDUCTOR}} = 4.7 \mu\text{H}$  - diameter = 4.5 mm



Figure 4.  $L_{\text{INDUCTOR}} = 4.7 \mu\text{H}$  - diameter = 5.8 mm



Figure 5.  $L_{\text{INDUCTOR}} = 4.7 \mu\text{H}$  - diameter = 7.8 mm (STMicroelectronics reference design: ANT3-M24LR-A)

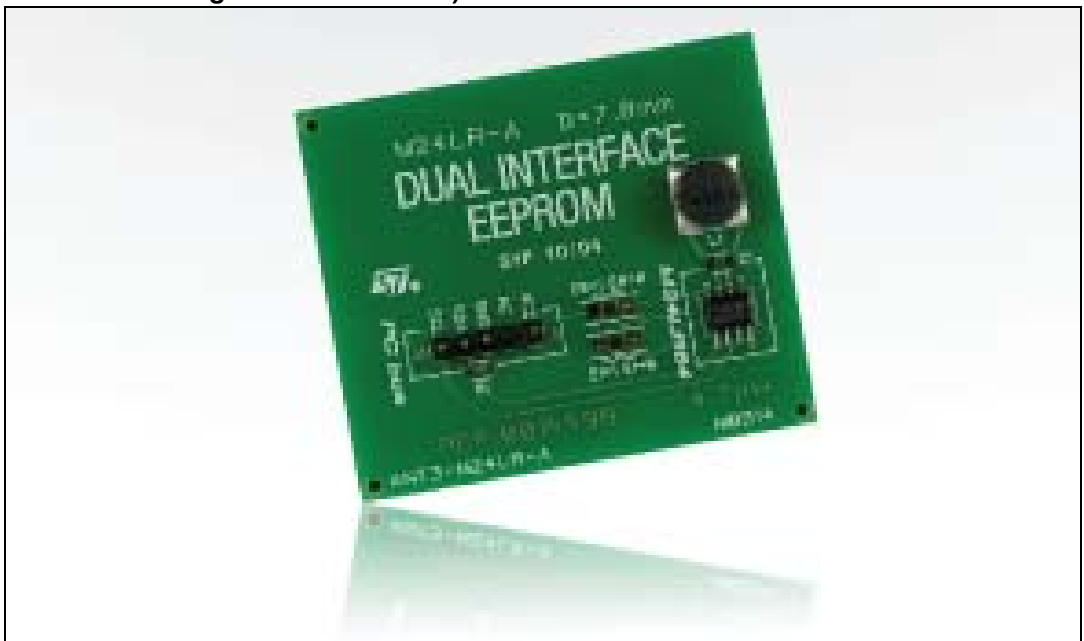


Figure 6.  $L_{\text{INDUCTOR}} = 4.7 \mu\text{H}$  - diameter = 9.8 mm





## 5 Read range considerations


The read range is the maximum distance between an RF reader and the M24LRxx antenna.

First and foremost, you must choose the right inductor value so that the resulting antenna is properly tuned to your application.

However, for a given inductance value, the read range varies depending on the actual size of the inductor. The bigger the inductor, the bigger the active surface of the inductance, the more energy and data are captured by the M24LRxx devices and the better the read range.

To illustrate this, ST has measured the effect of various sizes of inductor on the ANT3-M24LR64 reference antenna, using a Feig MR101 ISO15693 reader. The inductance value is the same for all inductors: 4.7  $\mu\text{H}$ .

**Figure 7. Read range (cm) vs inductor diameter (mm) using a Feig MR101 reader**

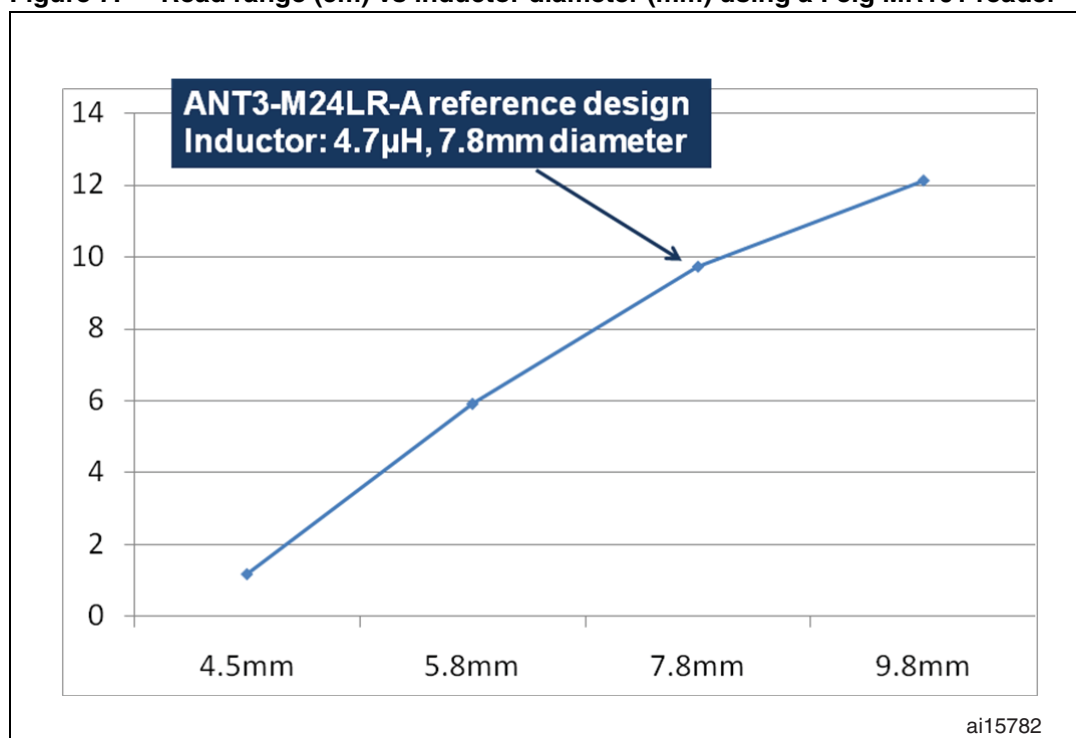

## 6 Revision history

**Table 2. Document revision history**

Date	Revision	Changes
15-Mar-2010	1	Initial release.
19-Jul-2010	2	Corrected document number in page headers.

**Please Read Carefully:**

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

**UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.**

**UNLESS EXPRESSLY APPROVED IN WRITING BY TWO AUTHORIZED ST REPRESENTATIVES, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.**

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2011 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

[www.st.com](http://www.st.com)

